

# 605.204 - Computer Organization

## Module 13: Assignment

Nick Hinke

December 4, 2022

### **Brief Introduction**

This assignment involves the implementation of several modulo counters within various Logisim circuits. All of my resulting work can be found at this *GitHub link* and can be cloned and viewed using the following commands:

```
git clone https://github.com/nhinke/computer-organization-repo.git
cd computer-organization-repo/assignments/module13/
```

## Problem 1

1. Implement the following state diagram using the mod-4 counter as a starting point.

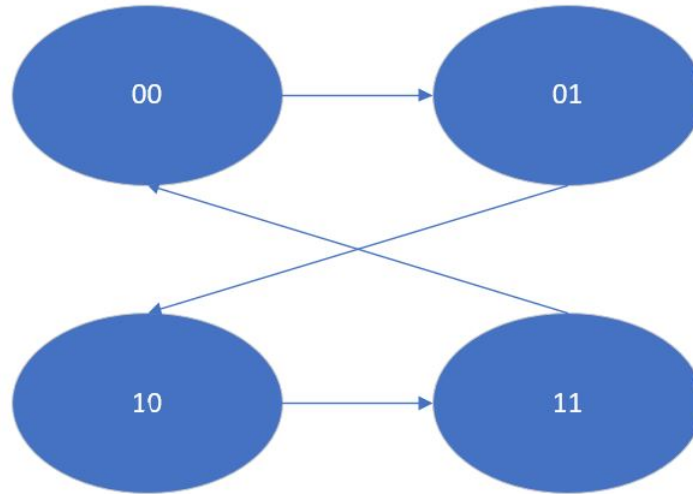


Figure 1: Screenshot of state diagram to be implemented using mod-4 counter

Circuits used to implement state diagram above are shown on the following page...

Final Circuit:

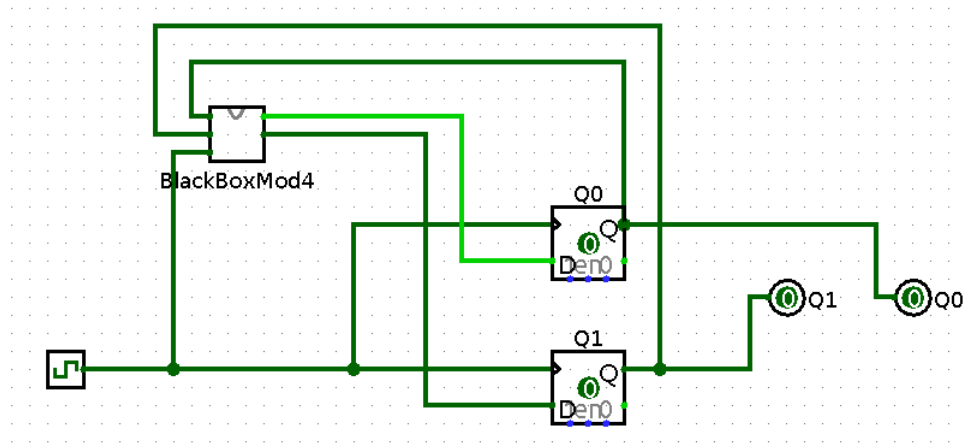


Figure 2: Screenshot of final circuit to implement state diagram

BlackBoxMod4:

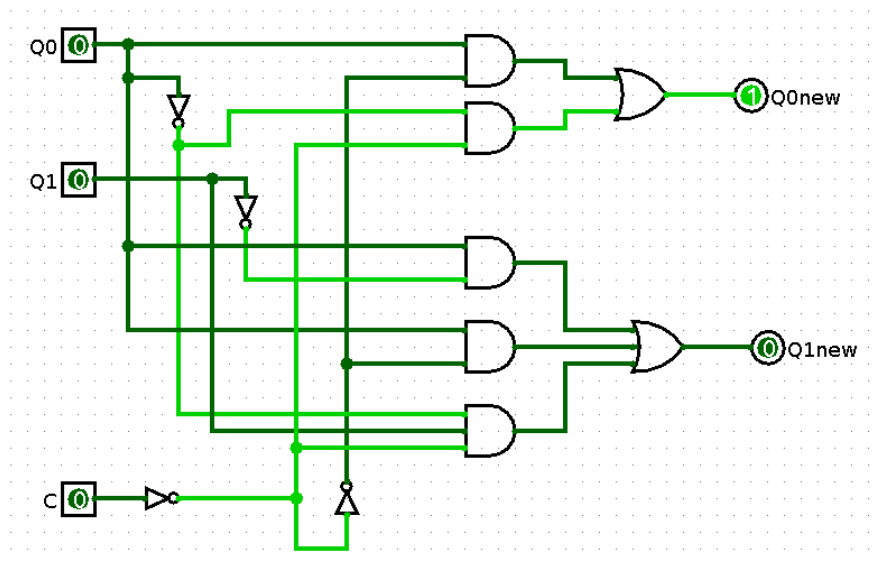


Figure 3: Screenshot of “BlackBoxMod4” circuit used within final circuit

## Problem 2

2. Implement a Mod-6 counter using 3 registers and a 6x3 ROM memory.

Final Circuit:

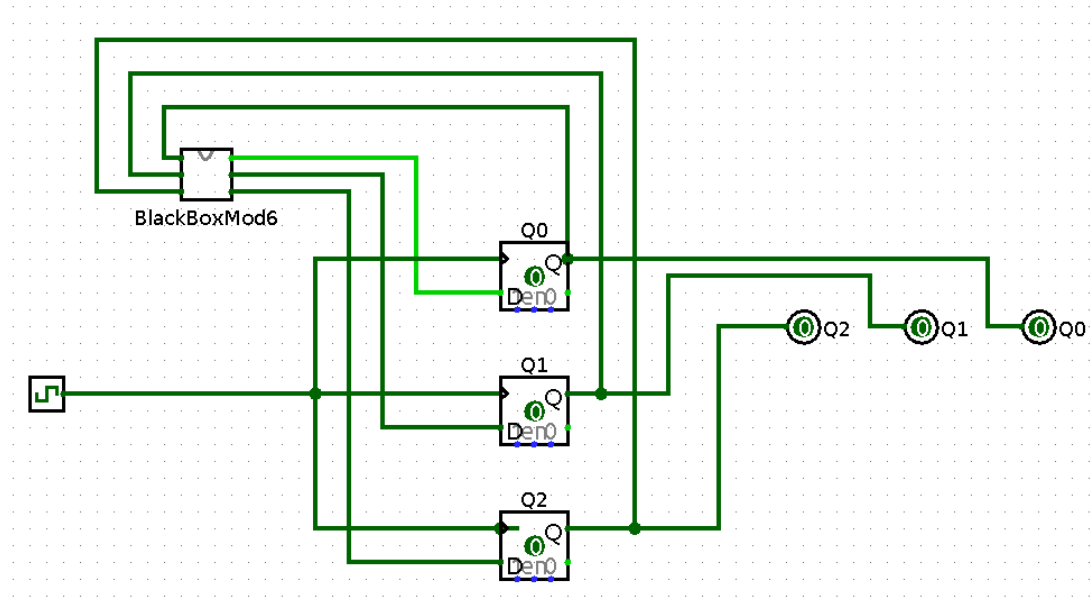


Figure 4: Screenshot of final circuit to implement mod-6 counter

BlackBoxMod6:

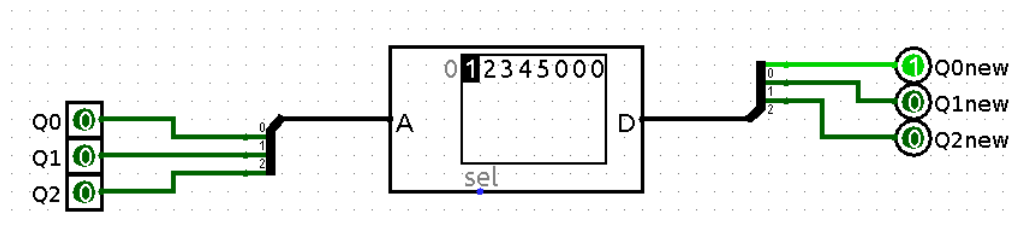


Figure 5: Screenshot of “BlackBoxMod6” circuit used within final circuit